

Andrew Smit

ECE 5330

10/15/18

Pre-Lab Questions for Lab4

1. Based on the electrical characteristics of the NUC140 (see the TRM), given that $V_{DD}=4.5V$ what is the source current for (PA, PB, PC, PD, PE) when in quasibidirectional mode?

The source current is a minimum of $-300\ \mu A$, typically $-370\ \mu A$, and a max of $-450\ \mu A$ given that $V_{DD} = 4.5V$ and in quasibidirectional mode.

What is the sink current ($V_{DD}=4.5V$) for (PA, PB, PC, PD, PE) in quasibidirectional mode?

The sink current is a minimum of 10 mA, typically 16 mA, and a max of 20 mA given that $V_{DD} = 4.5V$ and in quasibidirectional mode.

2. How much current can the ports source and sink in the push-pull mode when $V_{dd}=4.5\ V$.

The source is a minimum of -20 mA, typically -24mA, and max of -28mA. The sink is the same as the quasibidirectional mode which is a minimum of 10 mA, typically 16mA, and max of 20 mA.

3. Derive the values for R2 and R3 in Figure 1 as defined previously in the lab handout. If you do this via Matlab or Maple, please include the results and the code used.

```
% Find R2 and R3 values
R1 = 1000;
syms R2;
syms R3;
Vs = 2.64;
VDD = 3.3;

VA = 0.3*Vs;
R3 = solve(par(R1,R3)*VDD/(par(R1,R3)+R2)-VA,R3);

VA2 = 0.7*Vs;
R2 = solve(par(R1,R2)*3.3/(par(R1,R2)+R3)-VA2,R2);
R2 = double(R2)

syms R3;
```

```
R3 = solve(par(R1,R3)*VDD/(par(R1,R3)+R2)-VA,R3);  
R3 = double(R3)
```

This Matlab code solves for R_2 and R_3 . It gives values of $R_2 = 833.33\Omega$ and $R_3 = 357.143\Omega$. The following code checks these values to make sure the appropriate V_A voltages.

```
R1 = 1000;  
R2 = 833.3333;  
R3 = 357.1429;  
  
VDD = 3.3;  
Vs = 2.64;  
  
VA0 = par(par(R1,R2),R3)*0/Vs  
VA1 = par(R1,R3)*VDD/(par(R1,R3)+R2)/Vs  
VA2 = par(R1,R2)*VDD/(par(R1,R2)+R3)/Vs  
VA3 = R1*VDD/(par(R2,R3)+R1)/Vs
```

The output window shows $V_{A0} = 0.0$, $V_{A1} = 0.30$, $V_{A2} = 0.70$, and $V_{A3} = 1.0$